

14th August
2021

-: Chapter 14 :-

DATE: / 20
PAGE NO:

Semiconductor Electronics: Materials, Devices and Simple Circuits

→ Classification of Material

- ① Conductor \rightarrow Fully allows electric current $\frac{I}{R} \propto E$
- ② Insulator $R = R_0(1 + \delta \frac{1}{T})$
 $\delta \uparrow \text{Resistance} \uparrow$
- ③ Semiconductor \rightarrow

→ Does not allow flow of charges easily

(Conductivity lies between conductor and insulator)

$\delta = -ve \rightarrow \uparrow \text{Resistance} \downarrow \text{or}$

conductivity \uparrow
It's used in controlling flow of charges.

→ Energy Bands in Solids

Based on Pauli's Exclusion principle.


In an isolated atom electrons present in energy level but in solid, atoms are not isolated. Therefore interaction among each other due to this energy level shifted into different

energy levels. Quantity of those


different energy levels depends on the quantity of interacting atoms. Splitting of sharp and closely compact energy levels result into energy bands. This is discrete in nature.


Energy Band Diagram:-

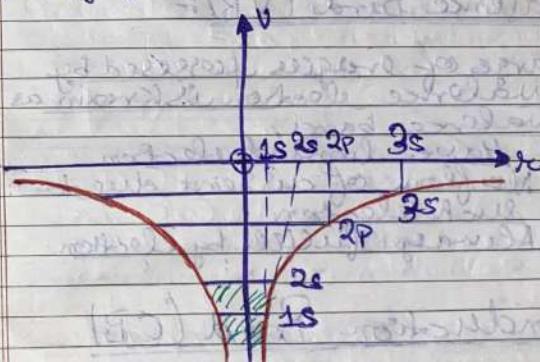
Potential energy of $e^- \rightarrow V = \frac{k_e(z)}{r}$



-: For Single atom :-

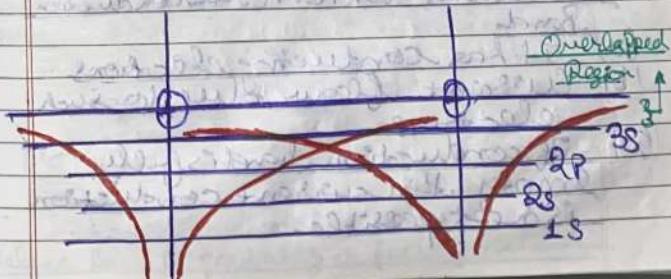

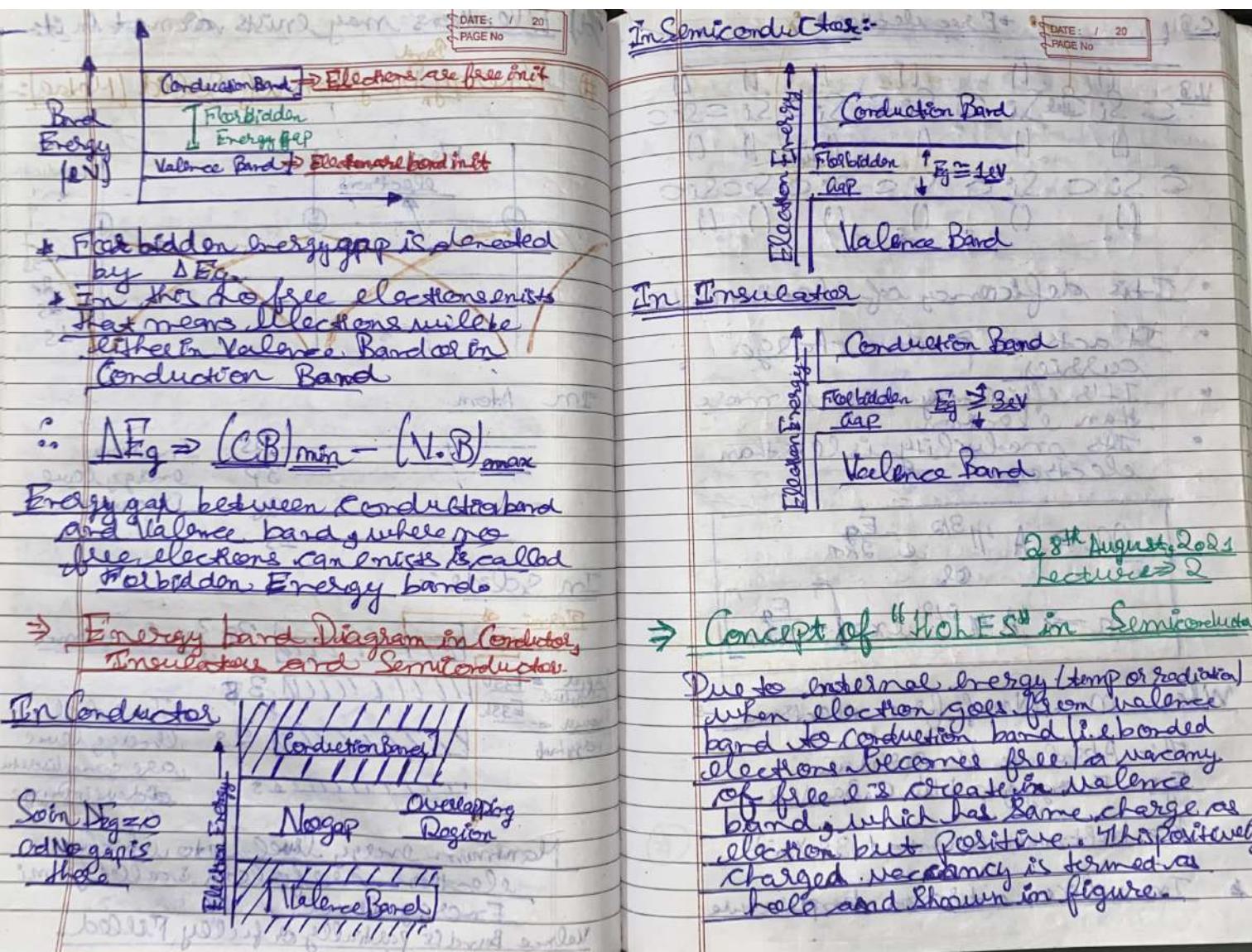

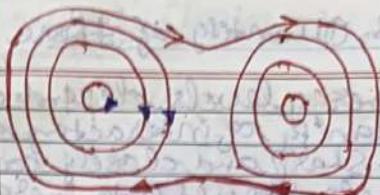

DATE : / / 20
PAGE NO:

∴ Energy band :- Range of energy possessed by electron in a solid is known as energy bands.

∴ Valence Band (VB) :-

Range of energies possessed by valence electrons is known as valence band.

- Have fixed electron
- No flow of current due to such electron
- Always full by electron


∴ Conduction Band (CB)

Range of energies possessed by free electrons is known as conduction band.


- It has conducting electrons
- Current flows due to such electrons
- If conduction band is fully empty then current conduction is not possible.

(d) Electrons may exists unoccupied in its band


Energy Diagram of Solid (Metal) :-

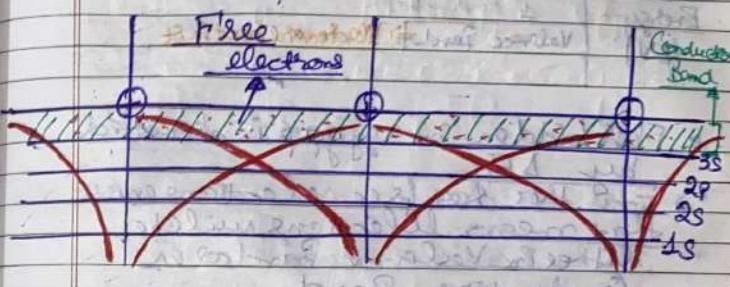

In Atom

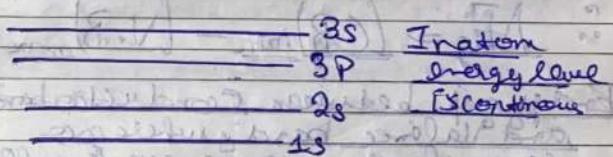


In Solid :-

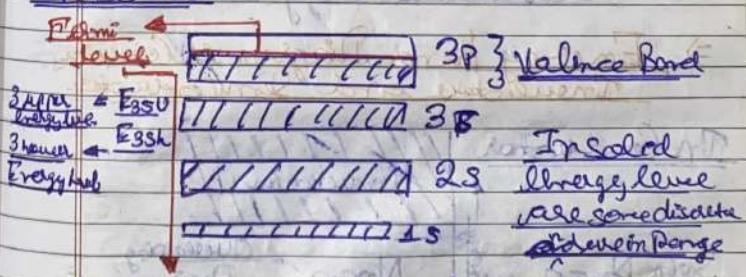

Fermi level
Superconductor
3s E_{35U}
3p E_{35H}
Fermi level

Non-metals
Metals
Conductors
Insulators

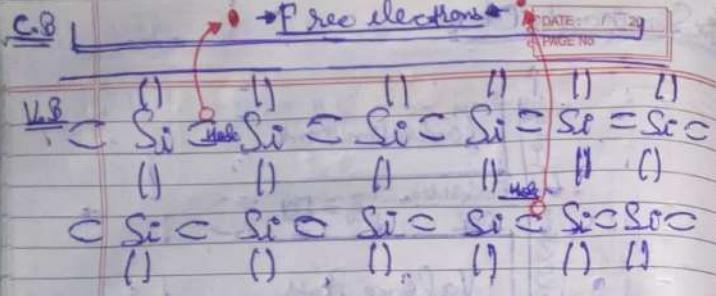Valence Band is partially or fully filled.



- It is deficiency of electron in V_{AB}
- It acts as positive charge carrier
- Its efficiency mass is more than electron
- Its mobility is less than electron

$$n \Rightarrow A \gamma^{3/2} e^{-\frac{E_g}{2kT}}$$

$$n \Rightarrow A \gamma^{3/2} \exp\left[-\frac{E_g}{2kT}\right]$$

Where n = No. of free electrons e^{-s}

T: Absolute Temperature

E_g : Energy gap b/w C.B and V_{AB}


k = boltzmann constant $= 1.38 \times 10^{-23}$

In silicon at room temperature

out of 10^{12} Si atoms only one electron

goes from V_{AB} to C_{CB}.


* In germanium at room temperature out of 10^9 Ge atoms only one electron goes from V_{AB} to C_{CB}.
 → Free conductivity > Si conductivity

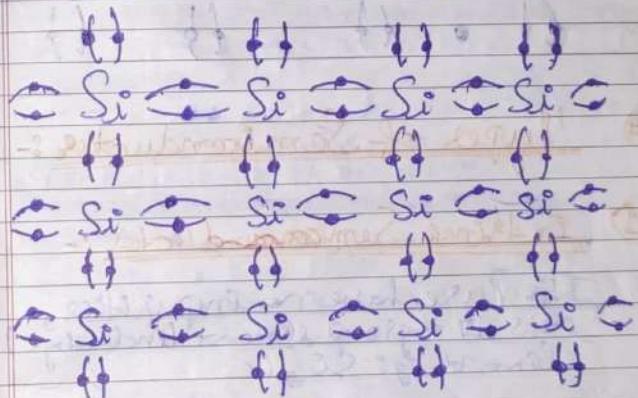

at 0K
 Valence band fully filled and
 conduction band fully empty

⇒ It will behave as perfect Insulator

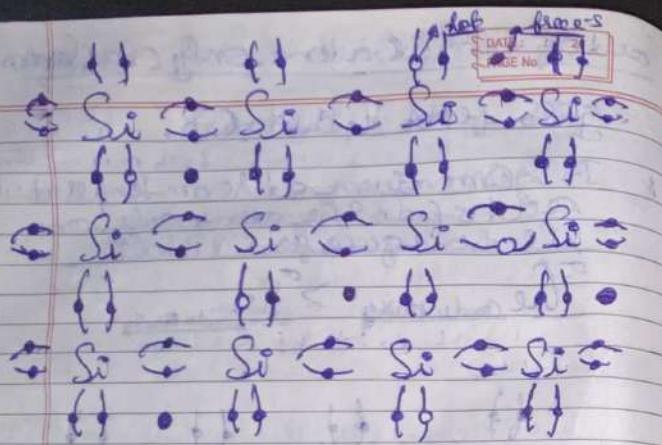At high temperature
 Valence band partially empty, conduction band partially filled
 ⇒ Poor Conductor → It Behaves



Types of Semiconductors :-

① Intrinsic Semiconductor :-

It's pure have no impurities.
It's IV th group element (including)
element e.g.: Si, Ge

$$(\Delta E_g)_{Si} = 1.1 \text{ eV} \quad (\Delta E_g)_{Ge} = 0.7 \text{ eV}$$

② Extrinsic Semiconductors

It has desired impurity also
called as Doping and this
Type of semiconductor is called
Doped Semiconductor.

If doping is done of III rd group then

This semiconductor is called \rightarrow p-type semiconductor.


And if it is doped wth group (V or VI) then
it is called \rightarrow n-type Semiconductor

[to increase conductivity]

[The particle which we are adding are
called Dopeants]

- The impurity added may be \approx 1 part per million (ppm).
 - The dopant atom should take the position of semiconductor atom in the lattice.
 - The size of the dopant atoms should be almost the same as that of the crystal atom.
 - The presence of the dopant atom should not disturb the crystal lattice.
- \Rightarrow Doping of a semiconductor increases its electrical conductivity to a great extent.

③ Intrinsic SiC Semiconductor

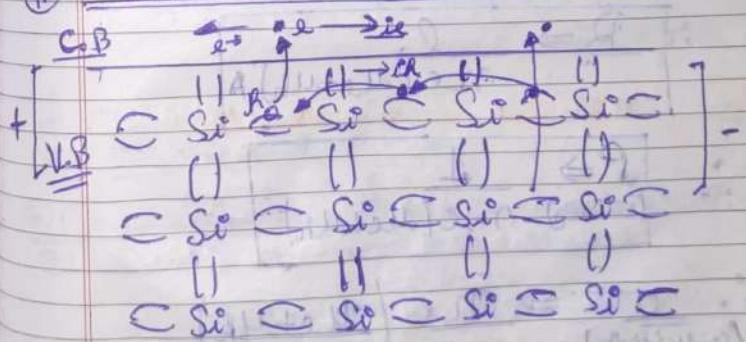

Appion 108. Solutions contribute

more e-h pair and if it is p-type Semiconductor then $N_e = N_h = N_i = n$

When n = Number density
 n_i = No. of intrinsic carriers / volume

$i \Rightarrow i_e + i_h$ is Net current

① Current in P-type Semiconductor

$$V_d \rightarrow D.P.E. \quad i \Rightarrow i_e + i_h$$

$$V_d \rightarrow V_F \quad i \Rightarrow n_e i A (V_d) e + n_h i A (V_d) e$$

$$n_e = n_i e^n$$

$$\mu_e = \mu_{h,i}$$

$$i \Rightarrow n_e A \mu_e V_d + n_h A \mu_h V_d$$

$$E = \text{Electric Field} \quad \frac{V}{R} \Rightarrow n_e A \mu_e V_d + n_h A \mu_h V_d$$


$$R \Rightarrow \frac{l}{n_e (\mu_e + \mu_h) A}$$

$$P \Rightarrow \frac{1}{n_e (\mu_e + \mu_h)}$$

$$\sigma \Rightarrow n_e (\mu_e + \mu_h)$$

Extrinsic Semiconductor

(a) N-type (18th Group)

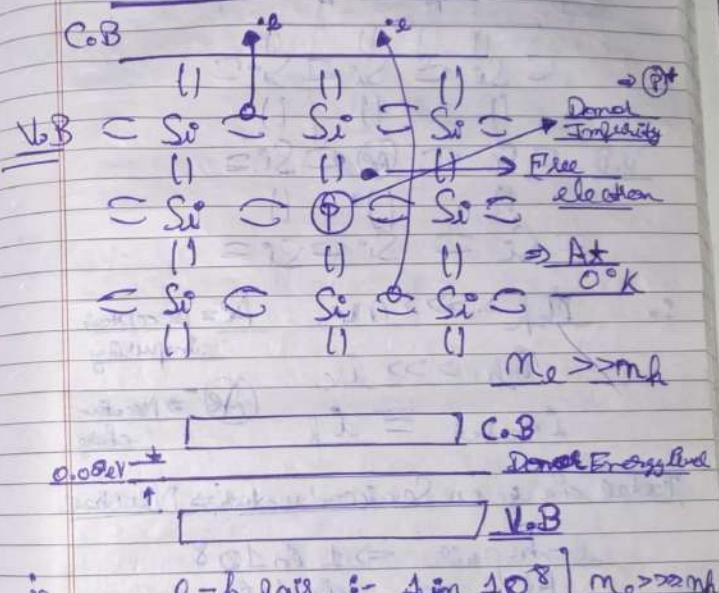


$e-h$ pair :- $1 \text{ in } 10^8$ $n_e > n_h$
 Impurity :- $1 \text{ in } 10^6$ $\Rightarrow e > h$


$h \Rightarrow$ Minority Charge carrier
 $e \Rightarrow$ Majority charge carrier

$i \text{ in } Si$

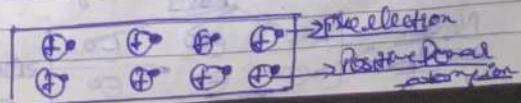② Overall charge on Semiconductor \Rightarrow Neutral
 ③ Donor atom \Rightarrow Positive



(b) P-Type Semiconductor [13th Group]

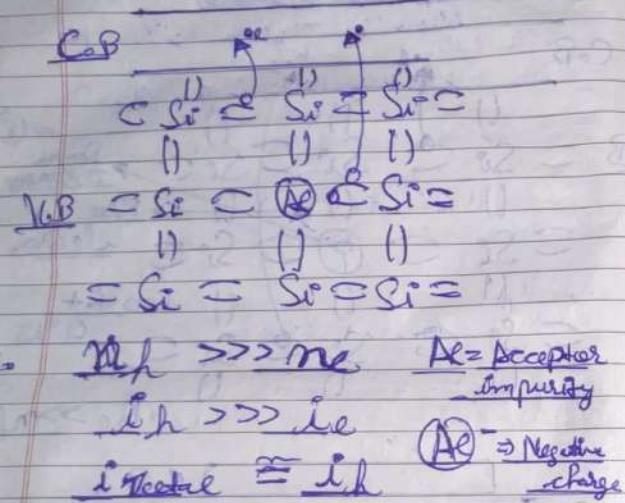


Total charge on Semiconductors \Rightarrow Neutral


$$l-h \text{ pair} \rightarrow 1 \text{ in } 10^8$$

$$A_e^- \rightarrow 1 \text{ in } 10^6$$

Majority charge carriers

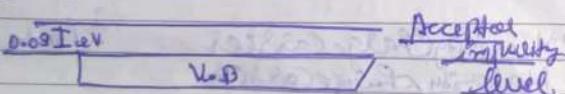

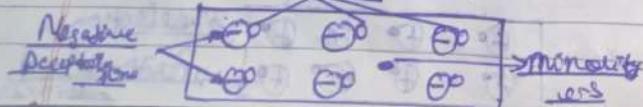$h \Rightarrow$ Majority charge carrier
 $l \Rightarrow$ Minority charge carrier



Note:-

Intrinsic Semiconductor
 $n_e = n_h \Rightarrow n_i^2$ [Mass action law]

P-type: Let Acceptor impurity concentration is N_A
 $\therefore n_h = n_e$
 $\therefore n_e = n_i^2$

N-type: Let Donor Impurity Concentration $\Rightarrow N_D$
 $\therefore n_e \rightarrow n_D$
 $\Rightarrow n_h \rightarrow n_i^2$

1: The mean free path of conduction electron in copper is about $4 \times 10^{-8} \text{ m}$. For a copper block find the electric field which can give an average energy to a conduction electron

Aus:-

$$\frac{\Delta E}{d} = \frac{1}{4 \times 10^{-8}}$$

$$(q/E)d \Rightarrow 1 \text{ eV}$$

$$E \Rightarrow 1$$

$$E \Rightarrow 2.5 \times 10^7 \text{ V/m}$$

2: Calculate Resistivity of an N-type semiconductor from the following

^{DATA}

density of conduction electron
 $\Rightarrow 8 \times 10^{13} \text{ cm}^{-3}$, density of holes
 $\Rightarrow 3 \times 10^{17} \text{ cm}^{-3}$, mobility of conduction electron $= 203 \times 10^{-4} \text{ cm}^2 \text{ V}^{-1} \text{ s}^{-1}$ and mobility of holes $= 100 \text{ cm}^2 \text{ V}^{-1} \text{ s}^{-1}$.

Ans 3:

$$P = \frac{1}{e \cdot n \cdot m \cdot h \cdot A}$$

∴

$$e \Rightarrow h$$

$$\therefore P = 0.34 \Omega \text{ m} \quad (\text{Ans})$$

- (a) A doped semiconductor has impurity levels 30 meV below the conduction band (a) Is the material n-type or p-type?
 (b) If a thermal relaxation energy K energy is given to the extra electron loosely bound to the impurity ion and this electron is just able to jump into the conduction band. Calculate the temperature T .

Ans 3: (a) Hence it is a doped Semiconductor is of n-type because it is just below the conduction band.

(b)

$$K = K_B = 30 \text{ meV} = 30 \times 10^{-3} \text{ eV}$$

$$T \Rightarrow \frac{30 \times 10^{-3}}{8.62 \times 10^{-5}} \Rightarrow 464 \text{ K} \quad (\text{Ans})$$

Q. The energy of a photon of sodium

light ($\lambda = 589 \text{ nm}$) equals the band gap of a semiconducting material. (a) Find the minimum energy E required to create a hole-electron pair. (b) Find the value of E/kT at a temperature of 300 K.

Ans 4: (a) Minimum Energy $\Rightarrow E = E_g = \frac{hc}{\lambda}$

$$\therefore E_g \Rightarrow \frac{6.62 \times 10^{-34} \text{ m}^2 \text{ kg/s}}{589 \times 10^{-9} \text{ m}} \times 3 \times 10^8 \text{ m/s}$$

$$E_g \Rightarrow 2.1 \text{ eV}$$

$$(b) \frac{E}{kT} \Rightarrow \frac{2.1 \text{ eV}}{8.62 \times 10^{-5} \times 300} \Rightarrow 81 \text{ (Ans)}$$

(c) A p-type semiconductor has acceptor levels 57 meV above the valence band calculate the maximum wavelength of light which can be absorbed.

Ans 5:

$$E = \frac{hc}{\lambda}$$

$$\therefore \lambda \Rightarrow \frac{6.6 \times 10^{-34} \times 3 \times 10^8}{57 \times 10^{-3} \times 1.6 \times 10^{-19}}$$

$$\lambda \Rightarrow 0.2171 \times 10^{-4} \text{ m}$$

$$\lambda \Rightarrow 2.18 \times 10^{-7} \text{ m} \quad (\text{Ans})$$

62

The bandgap in germanium

is $\Delta E = 0.68 \text{ eV}$. Assuming that the number of hole-electron pairs is proportional to $e^{-\Delta E/2kT}$ find the percentage increase in the number of charge carriers in pure germanium at the temperature increased from T_1 to T_2 .

$$\text{Ans} \rightarrow \text{bandgap} \Rightarrow \Delta E = 0.68 \text{ eV}$$

Let N_1 = Number of charge carriers

at T_1

And N_2 = Number of charge carriers

at T_2

$$N_1 = N_{\text{e}} e^{-\Delta E/2kT_1}$$

$$\therefore N_2 = N_{\text{e}} e^{-\Delta E/2kT_2}$$

$$\% \text{ increase} \Rightarrow \frac{N_2 - N_1}{N_1} \times 100$$

$$\% \text{ increase} \Rightarrow \frac{N_{\text{e}} (e^{-\Delta E/2kT_2} - e^{-\Delta E/2kT_1})}{N_{\text{e}} e^{-\Delta E/2kT_1}}$$

$$\% \text{ increase} \Rightarrow e^{-\Delta E/2kT_2} - e^{-\Delta E/2kT_1}$$

$$\% \text{ increase} \Rightarrow \left[\frac{e^{-\Delta E/2kT_2}}{e^{-\Delta E/2kT_1}} - 1 \right] \times 100$$

$$\% \Rightarrow e^{\frac{\Delta E}{2k} \left[\frac{1}{T_2} - \frac{1}{T_1} \right]} - 1$$

$$\% \Rightarrow \left(e^{\frac{0.68 \times 10^{-3}}{2 \times 8.62 \times 10^{-5}} \left[\frac{1}{300} - \frac{1}{320} \right]} - 1 \right)$$

$$\% \Rightarrow 100 \left[e^{0.27} - 1 \right] \rightarrow 100 \times 1.27$$

$$\% \Rightarrow 127 \text{ (Answer)}$$

72

The concentration of hole-electron pairs in pure silicon at $T_1 = 300 \text{ K}$ is $4 \times 10^{15} \text{ per cubic centimetre}$. Antimony is doped into silicon in proportion of 1 atom to 10^{17} atoms. Assuming that half of the impurity atoms contribute electrons in conduction bands, calculate the factor by which the number of charge carriers increases due to doping. The number of silicon atoms per cubic metre is 8×10^{28} .

Ans: The number of charge carriers before doping = Number of holes + number of charge carriers $\Rightarrow 2 \times 10^{15} \times 2 \rightarrow 1.4 \times 10^{15} \text{ cm}^{-3}$

Since antimony is doped in the proportion of 1 in 10^{17} atoms.

$$\text{No. of antimony atoms} \rightarrow \frac{1}{10^{17}} \times 8 \times 10^{28}$$

$$\rightarrow 8 \times 10^{11}$$

As half of these atoms contribute

electrons to the conduction band

Now if entire conduction electrons
 $\Rightarrow 2.5 \times 10^{21}$

The factors which need charge

increased $\Rightarrow 2.5 \times 10^{21}$
 14×10^{15}

$$\Rightarrow 1.8 \times 10^8 \text{ Ans}$$

Q8: A strip of copper or another
of germanium is cooled
from room temperature to
Boyle's temperature of:-

Ans 8: Copper is conductor and germanium
is semiconductor so when
cooled:-

Resistance of copper strip decreases
and that of germanium increases

Q9: The forbidden energy bandgap
in conductors, semiconductors
and insulators are E_{h_1} , E_{h_2} and
 E_{h_3} respectively. The relation
among them is:-

$$\text{Ans 9: } E_{h_3} > E_{h_2} > E_{h_1}$$

10: The valence band at 0 K is

Ans 10: (A) Completely filled

Electric conduction in semiconductor
takes place due to:

Ans 11: Both electrons and holes

12: An electric field is applied to
a semiconductor. Let the number
of charge carriers be n and
average drift speed be v . If the
temperature is increased.

Ans 12: So: drift Speed & Deltastation time

So: n will increase and v will decrease

13: P-type semiconductor is formed
when

Ans 13: B: Al impurity is mixed in Si
C: B impurity is mixed in Ge.

14: In an intrinsic semiconductor

Ans 14: The gap between conduction
band and valence band is nearly
about 1 eV.

15: The free electron concentration (n)
in the conduction band of a
semiconductor at a temperature
 T Kelvin is described in terms of
 E_g and k as $n = A T^n e^{-E_g/2kT}$ where

$$\text{Ans 15: } n \Rightarrow \frac{3}{2} \Rightarrow 1.5 \text{ (From Fermi)}$$

Q16: The mobility of electrons and holes in a sample of intrinsic germanium at room temperature are $0.36 \text{ cm}^2/\text{V}\cdot\text{s}$. If electron and hole densities each are equal to $2.8 \times 10^{19}/\text{m}^3$, the conductivity of germanium will be ohm-metre.

$$\text{Ans 16: } O \Rightarrow \frac{1}{P} = e(4eV_e + 4eV_h)$$

$$O \Rightarrow \frac{1.6 \times 10^{-19}}{2.8 \times 10^{19}} (0.36 + 0.14)$$

$$O \Rightarrow 5 \text{ nm}$$

Q17: In a P-type semiconductor, the acceptor level is 0.2 eV above the valence band. If the minimum wave length (λ_0) of light required to produce a hole will be

$$\text{Ans 17: } E \Rightarrow hc \cdot \frac{1}{\lambda} \Rightarrow 2$$

$$\lambda \Rightarrow 1.240 \text{ eV} \times 10^{-6}$$

$$\lambda \Rightarrow 1000 \text{ A} \Omega \text{ (Ans)}$$

Q18: A P-type silicon semiconductor is made by adding an atom of indium per 5×10^7 atoms of silicon. The mobility of electrons and holes in a sample of intrinsic germanium at room temperature are $0.36 \text{ cm}^2/\text{V}\cdot\text{s}$. If electron and hole densities each are equal to $2.8 \times 10^{19}/\text{m}^3$, the conductivity of germanium will be ohm-metre.

Silicon is $2.8 \times 10^{28} \text{ atom/m}^3$. If there are acceptor atoms in per cubic cm of silicon is $5 \times 10^7 \text{ atoms/cm}^3$.

Then find:-

$$\text{Ans 18: } 1 \text{ Indium} \Rightarrow 5 \times 10^7 \text{ Si}$$

$$\frac{1}{5 \times 10^7} \text{ I} \Rightarrow 1 \text{ Si}$$

$$\text{So: } \frac{25 \times 10^{28} \text{ atom/m}^3}{5 \times 10^7} \Rightarrow 25 \times 10^{28} / \text{m}^3$$
$$\Rightarrow \frac{25 \times 10^{28}}{5 \times 10^7} \times 10^{-6} / \text{cm}^3$$

$$\text{Ans} \Rightarrow 5 \times 10^{18} \text{ Im atom/cm}^3$$

$$\text{So: } M \Rightarrow 5$$

Q19: If the conductance of pure silicon crystal at room temp is $7 \times 10^{-6} \text{ mho/cm}$. Find electron hole pair per cm³ is $5 \times 10^{10} / \text{cm}^3$ at this temp. $n_p = 1.3 \times 10^{10} \text{ cm}^2 / \text{volt sec}$ and $n_h = 4.8 \times 10^{10} / \text{volt sec}$

$$\text{Ans 19: } So \Rightarrow n_p \Rightarrow 1.072 \times 10^{10}$$

$$O \Rightarrow n_e e M + n_h h M$$

$$O \Rightarrow n_e e (M + M)$$

$$O \Rightarrow 1.072 \times 10^{10} \times 1.6 \times 10^{-19} / (\text{volt sec})$$

$$n_h = 1.25 \times 10^{10} \text{ cm}^{-3}$$

$$n_h = \frac{q}{l} \times 10^{10} \text{ cm}^{-3}$$

$$\frac{5}{q} \Rightarrow \frac{1.25 \times 10^{10}}{100}$$

$$l = 5 \text{ cm} \quad \boxed{\text{Ans}}$$

23. Pure Si at 300 K has square electron (holes) concentration of $1.5 \times 10^{16} \text{ m}^{-3}$. Doping by indium increases n_h to $4.0 \times 10^{22} \text{ m}^{-3}$. If no is increased to $5 \times 10^{19} \text{ m}^{-3}$. Find.

$$n_e n_h = n_i^2 \quad \text{--- (1)}$$

$$n_e' n_h \Rightarrow n_i^2 \quad \text{--- (2)}$$

$$\therefore n_e' n_h \Rightarrow 1$$

$$\frac{1.5 \times 10^{16} \times 1.5 \times 10^{16}}{5 \times 10^{19} \times 1.5 \times 10^{16}} = n_e' \times \frac{4.0 \times 10^{22}}{5 \times 10^{19}}$$

$$\frac{5 \times 10^{15} \times 10^{16}}{10^{22}} \Rightarrow n_e'$$

$$5 \times 10^{19} \text{ m}^{-3} \Rightarrow n_e'$$

$$\therefore \boxed{5 \text{ Ansver}}$$

4. The length of a germanium rod

is 0.58 cm and its area of cross section is 1 mm^2 . The germanium $n_i = 2.5 \times 10^{14} \text{ m}^{-3}$, $\mu_e = 0.19 \text{ m}^2/\text{V}\cdot\text{s}$, $\mu_h = 0.39 \text{ m}^2/\text{V}\cdot\text{s}$. Find the resistance of the rod (in k Ω)

Ans

$$R \Rightarrow l$$

$$n_e = 5 (\text{Ans})$$

$$R \Rightarrow \frac{0.58 \text{ cm} \times 10^{-2}}{2.5 \times 10^{14} \times 1.6 \times 10^{-16} (\text{Ans})}$$

$$R \Rightarrow 2.5 \text{ k}\Omega$$

25. The contribution of the total current flowing through a semiconductor due to electrons and holes are $\frac{3}{4}$ and $\frac{1}{4}$ respectively. If the drift velocity of electrons is 5 times that of holes at this temperature. If the ratio of the concentrations of electrons and holes is 5. Find

$$\text{Ans} 20\% \quad \text{When } I_d \Rightarrow \frac{3}{4} \quad I_R \Rightarrow \frac{1}{4}$$

$$I_d \Rightarrow \frac{S}{2} Vd$$

$$I = n e A Vd$$

$$I_d \Rightarrow n_e l A \times Vd \quad \text{--- (1)}$$

$$\sigma \Rightarrow 1.6 \times 10^{-19} \times 1.622 \times 10^{-10}$$

$$= 1.830$$

$$\sigma \Rightarrow 3.14 \times 10^{-6} \text{ mho/cm}$$

$$\sigma \Rightarrow 2 \times \pi \times 10^{-6} \text{ mho/cm}$$

$$\therefore n = 1 \text{ (Answer)}$$

Q20: For hidden energy gap of FeSi is 0.8 eV , maximum wave length of incident radiation for producing electron-hole pair in germanium semiconductor (in nm) is:

$$E \Rightarrow 0.8 \text{ eV}$$

$$\lambda_{\text{max}} \Rightarrow \frac{62.34}{0.8} \times 10^{-10}$$

$$\lambda_{\text{max}} \Rightarrow 7.75 \times 10^3$$

$$\lambda_{\text{max}} \Rightarrow 7.75 \times 10^3$$

Q21: Mobility of electron in N-type Ge is $3000 \text{ cm}^2/\text{volt}\cdot\text{sec}$ and conductivity 18 mho/cm^2 . If effect of holes is negligible and impurity concentration is $25 \times 10^{18} / \text{cm}^3$. Find y .

$$\mu_e \Rightarrow 3000 \text{ cm}^2/\text{volt}\cdot\text{sec}$$

$$\sigma \Rightarrow 18 \text{ mho/cm}^2$$

$$So: \sigma \Rightarrow n \epsilon (\text{measured})$$

$$S \Rightarrow 1.6 \times 10^{-19} \times n / (3000 \text{ cm}^2/\text{sec})$$

$$\frac{\sigma}{1.6 \times 10^{-19} \times 3000} \Rightarrow m$$

$$\therefore m \Rightarrow 6.25 \times 10^{19} \text{ cm}^{-3}$$

$$\therefore M \Rightarrow \frac{6.25}{100} \times 10^{15} \text{ cm}^{-3}$$

$$m = \frac{25}{Y} \times 10^{15} \text{ cm}^{-3}$$

$$\frac{25}{Y} \Rightarrow \frac{6.25}{100} \Rightarrow Y \Rightarrow 04 \text{ (Ans)}$$

Q22: The intrinsic carrier density in germanium crystal at 300 K is $2.9 \times 10^{10} \text{ per cm}^3$. If the electron density in an N-type germanium crystal at 300 K is $0.5 \times 10^{17} \text{ per cm}^3$, the hole density (per cm³) in this N-type crystal at 300 K is $\frac{\sigma}{Y} \times 10^{10}$. Find Y .

$$n_e \times n_h \Rightarrow n_e^2$$

$$0.5 \times 10^{17} \times n_h \Rightarrow (2.9 \times 10^{10})^2$$

$$0.5 \times 10^{17} \times n_h \Rightarrow \frac{2.9 \times 10^{10}}{100} \times 10^{26}$$

$$n_h \Rightarrow 6.25 \times 10^{19} \text{ cm}^{-3}$$

$$I_h \Rightarrow n_h \times e \times A \text{ Volt}$$

DATE: 20
PAGE NO:

$$\frac{I_m}{I_h} \Rightarrow \frac{n_e}{n_h} \times \frac{V_{th}}{V_{th}}$$

$$\frac{3}{4} \times \frac{4}{1} \Rightarrow \frac{n_e}{n_h} \times \frac{5}{2} \frac{V_{th}}{V_{th}}$$


$$\text{So: } \frac{n_e}{n_h} \Rightarrow \frac{6}{5}$$

$$\text{Ratio: } \frac{6}{5} \\ = \frac{4}{4} \Rightarrow 6$$


29th August, 2021
Lecture - 3

or Semiconductor Diode or Crystal

Diode

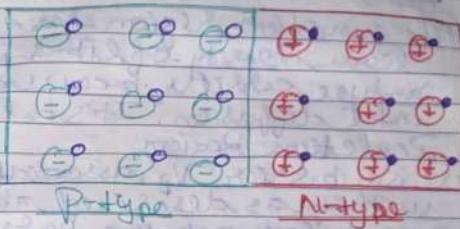

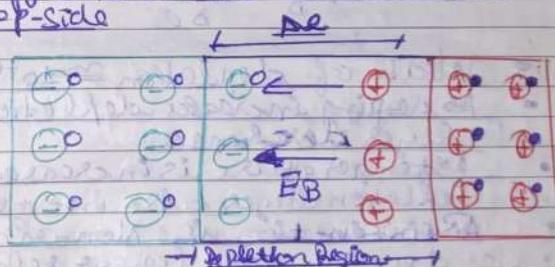In a p-n junction Diode, hole are majority carrier on p-side and electron on n-side. holes, thus diffuse to n-side and electrons to p-side.



This diffusion causes an excess positive charge in the n-region and an excess negative charge in p-region near the junction. This double layer of charge creates an electric field which hinders a flow both electrons and holes against their diffusion. In the equilibrium position, there is

P-N Junction

Techniques for Making P-N Junction

- (1) Alloy Method or Alloy Junction
 - (2) Diffusion Junction
 - (3) Vapour deposited junction or Epitaxial junction.
- When a P-type semiconductor is joined to an N-type semiconductor such that physical structure remain continuous at the boundary. The resulting arrangement is called P-N Junction Diode or

a barrier for charge movement
then-side at a higher
potential than the p-side.


- * The junction region has a very low density of either P or N-type carriers because of inter diffusion. It is called Depletion Region.

There is a barrier V_B associated with it as described above. This is called potential barrier.

In depletion layer: No free charge only fixed ones in this layer

$$F_B \rightarrow V_B \\ D.E.$$

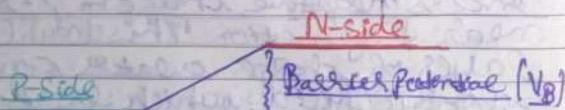- Width of depletion $\approx 10^{-6} \text{ m}$
- As doping increases depletion layer decreases.
- As temperature is increased depletion layer also increases
- P-N junction is Non-ohmic due to non-linear relation between I and V



V_B depends on (i) Doping Density (ii) Temperature

$$(V_B)_{Si} \Rightarrow 0.7 \text{ V} \quad (V_B)_{Ge} \Rightarrow 0.3 \text{ V}$$

$$\Delta V_B = -0.002 \text{ mV}$$

So on $\uparrow T \uparrow V_B \downarrow$ (Decreases)

① Representation of P-N Junction





∴ Because of concentration difference, holes try to diffuse from p-side to the n-side at the p-n junction. The diffusion give rise to a current from p-side to n-side called Diffusion current.

∴ Because of the thermal collisions, electron-hole pairs are created at every part of a diode. However, if an electron-hole pair is created in the depletion region, the electron is pushed by the electric field towards the n-side and the hole towards the p-side. This gives rise to a current from n-side to p-side called Hall current.


If there is no back diffusion, current = Drift current. So total current is zero.

Biasing of P-N Junction

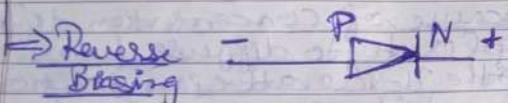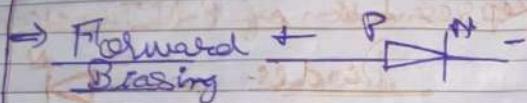Biasing \Rightarrow Study of application of electric difference across Diodes



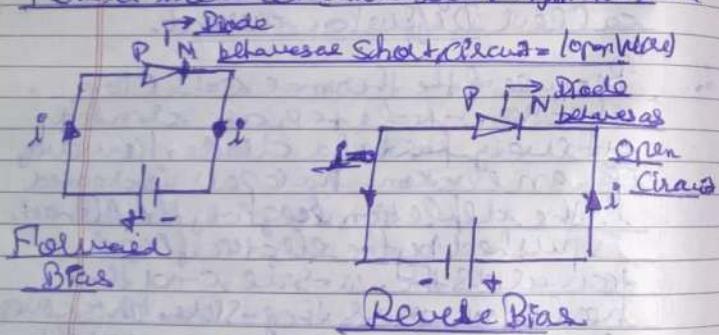No current condition i.e. P-N junction is open



Forward Bias

If we apply a voltage "V" such that P-side is positive and N-side is negative as shown in figure.

The applied voltage is opposite to

The junction barrier potential due to the effective potential barrier decreases, junction width also decreases. Some majority carrier will be allowed to flow across junction. It means the current flow is primarily due to majority charge carriers and it is in the order of ms called Forward Bias

F.B - Current flow due to majority charge carrier
 $i_{\text{diffusion}} > i_{\text{drift current}}$

So:- $i_{\text{net}} \Rightarrow$ Direction of Diffusion current i.e. from P \rightarrow N

Reverse Bias :-

If we apply a voltage "V" such that P-side is negative and N-side is positive as shown in Diagram. The applied voltage is in same direction as junction barrier potential. Due to this effective potential barrier increases junction width also increases. So no majority carrier will be allowed to flow across junction. Only minority carriers will be affected. It creates the current flowing primarily due to minority charge carriers


and is very small (in the order of μA).

This bias is called as Reverse Bias.

- In Reverse bias, the current is very small and nearly constant with bias (termed as reverse saturation current). If the reverse bias is increased further beyond a certain limit, above particular high voltage, breakdown of deflection layer started.

Zero Breakdown Avalanche Breakdown

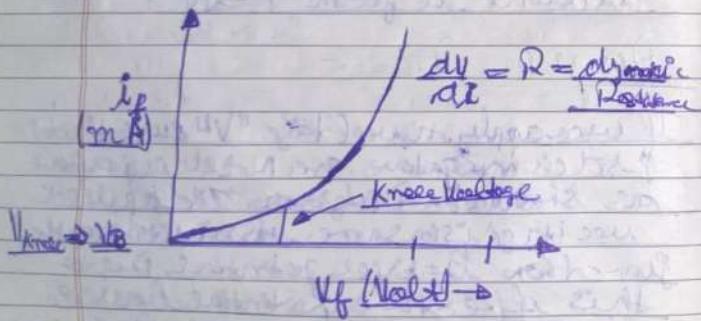
\Rightarrow Characteristic curve of Forward Bias



$$\text{Forward Resistance } R_f = \frac{V_f}{I_f} \Rightarrow \frac{V_f}{100\mu\text{A}} \approx 100\Omega$$

Order of Knee or cut-in Voltage
Ge $\rightarrow 0.3\text{V}$
Si $\rightarrow 0.7\text{V}$

\Rightarrow Characteristic curve of Bias

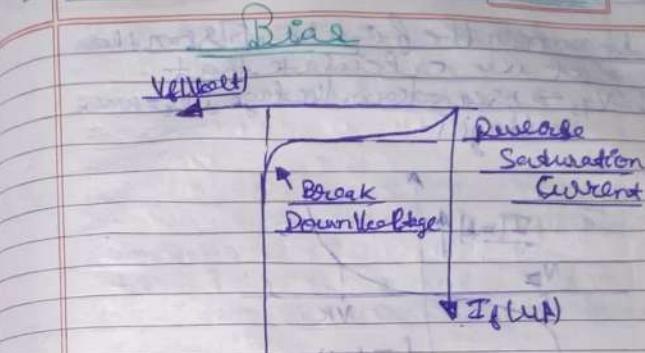

$$\text{Reverse Resistance } R_f \Rightarrow \frac{\Delta V_f}{\Delta I_f} \Rightarrow 10^6\Omega$$

Breakdown Voltage
Ge $\Rightarrow 20\text{V}$
Si $\Rightarrow 30\text{V}$

Q26: In a P-N Junction Diode not connected to any circuit:-

Ans: (c) There is an electric field with direction directed from N-type to P-type


Q27: When p-n junction diode is forward biased

Ans: (1) both the deflection regions and barrier height are reduced

Q28: The V-I characteristic for an p-n

junction Diode is plotted as

shown in the figure. From the plot we calculate that
 $V_D \rightarrow$ peak down voltage is V_K (reverse voltage)

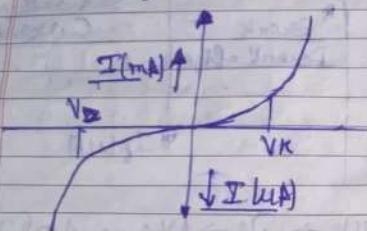

Ans 28: (1) The forward bias resistance is very high almost infinity for small values of V_{FD} and for the certain value it becomes very low.

(2) The reverse bias resistance of diode is very high in the beginning upto breakdown voltage is not achieved.

29: The depletion region of a P-N Diode, under open circuit condition contains

A 29: (C) Unashed immobile impurity ions

30:

Which is the wrong statement

The following sentence? A device in which P-N type Semiconductors are used is more useful than vacuum tube because:-

30a: (D) Its efficiency is high due to high voltage drop across the junction

31: Depletion layer of P-N junction is caused by

Ans 31: (B) Diffusion of free charge carriers

32: The contact potential at the junction site in a P-N junction is:-

Ans 32: (B) negative on P Side and Positive on N Side

33: When value of current increases in P-N junction, then the value of contact potential:-

Ans 33: (1) Decrease

34: In which case is the junction diode in reverse bias?

(1) +5V

(2) -10V

(3) 0V

(4) -2V

(1) -10V

(2) -2V


(3) 0V

(4) +5V


Ans 34: Soin F-B $V_D > V_B$

DATE: / /
PAGE NO:


Soin (B) option $V_D > V_B$

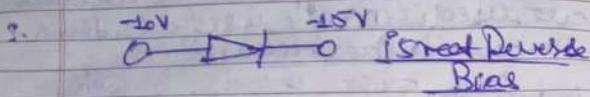

Ans 35: If V_D and V_B denote the potentials of A and B, then the equivalent between A and B will be adjoint electric circuit is.

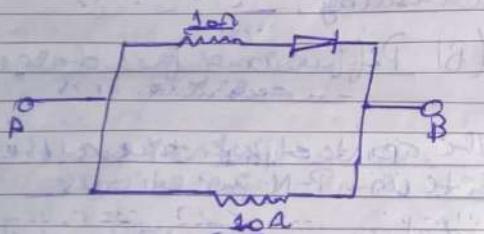

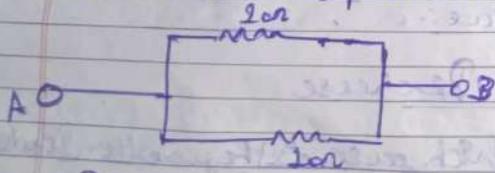Ans 36: Soin $I_D > I_B$ it means if in forward Bias and in this condition semiconductor behavior is open circuit.



$$R_{AB} \Rightarrow 8\Omega \text{ (In parallel)}$$

Ques 1/2) Soin in $V_D > V_B$

36f


'The Avalanche breakdown in P-N junction is due to :-'

Ans 36: (B) Cumulative effect of conduction band electron collision.

37: If the two ends of a P-N junction is joined by a wire:-

Ans 37: (A) There will meet a steady current onto circuit

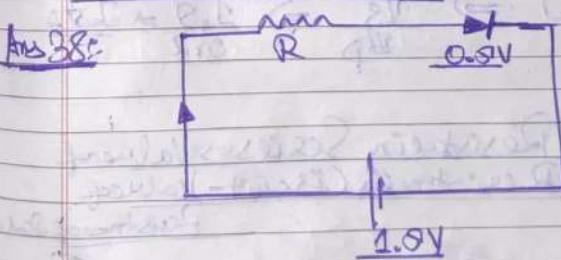38: The diode used in the circuit shown in the figure has a constant forward drop of 0.5V, a safe current and a maximum power rating of 100 milliwatts. What should be the value of the Resistor R (in ohm) connected in series with the diode for obtaining maximum current.



Voltage Drop across Diode (V_D) $\geq 0.5V$

Power maximum $P \Rightarrow 100 \text{ mW}$

$$P \Rightarrow 100 \times 10^{-3} \text{ W}$$

So Voltage of Source (V_s) $\Rightarrow 1.5 \text{ V}$

Resistance of Diode (R_D) $\Rightarrow \frac{V_D}{P}$

$$R_D \Rightarrow 0.5 \times 0.5 \\ 200 \times 10^{-3} \times 10 \times 10$$

$$R_D \Rightarrow \frac{25 \times 10^3}{10^4}$$

$$R_D \Rightarrow 2.5 \Omega$$

Current in Diode (I_D) $\Rightarrow \frac{V_D}{R_D}$

$$I_D \Rightarrow \frac{0.5}{2.5} \Rightarrow 0.2 \text{ A}$$


Note Resistance in circuit

$$(R) \Rightarrow \frac{V_s}{I_D} \Rightarrow \frac{1.5}{0.2} \Rightarrow 7.5 \Omega$$

\therefore Value of Resistor in Series \Rightarrow Value of Resistor in Circuit - Value of Resistance of Diode

Resistance in Series $\Rightarrow \frac{7.5 \Omega - 2.5 \Omega}{5 \Omega \text{ Ans}}$

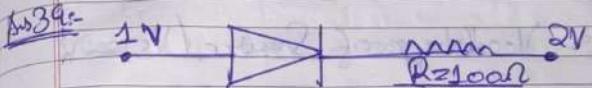Ans 39e In the arrangement shown in figure the current (in A) through ideal diode is:-



Since $V_B > V_D$ So it is in Reverse Bias and in ideal condition Reverse Bias behaves as Open circuit So Current \Rightarrow zero.


Ans 40e A diode made forward biased by a two volt battery however there is a drop of 0.5 V across the diode which is independent of current. Also a current greater than 10mA produces large junction loss and damages diode if diode is to be operated at 5mA. The series resistance in (R) to be put is:-

Ans 40e Voltage across Diode (V_D) $\Rightarrow 0.5 \text{ V}$

Current at which Diode is Operated $\Rightarrow (I_D) \Rightarrow 8 \text{ mA} = 8 \times 10^{-3} \text{ A}$

So Resistance of Diode (R_D) $\Rightarrow \frac{V_D}{I_D}$
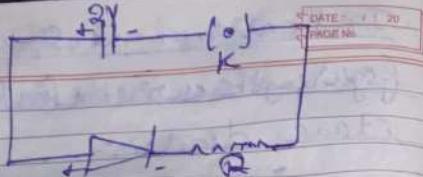
$$R_D \Rightarrow \frac{0.5}{8 \times 10^{-3}} \Rightarrow 62.5 \Omega$$



So. Need Voltage of Source (V_s) = 2V

$$\therefore \text{Resistance in Circuit } R \Rightarrow \frac{V_s}{I_D}$$


$$R \Rightarrow \frac{2}{5 \times 10^{-3}} \Rightarrow 400\Omega$$

Resistance in series $\Rightarrow R - R_D$


$$R_S \Rightarrow 400 - 100\Omega$$

$$R_S \Rightarrow 300\Omega \text{ (Ans)}$$

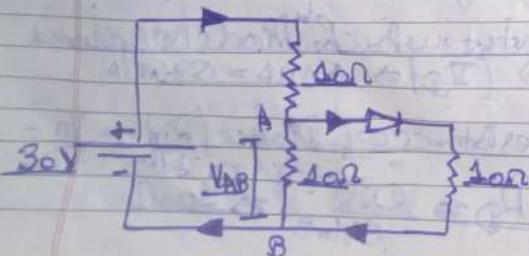Q1: Forming circuit to the potential difference V_{AB} (in V)



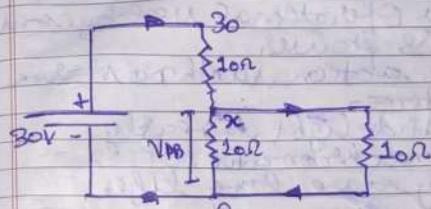Ans: Since Diode is forward biased
So it is considered as open straight wire.



$$\therefore \frac{n-30}{10} + \frac{n-0}{10} + \frac{n-0}{10} = 0$$

$$3n \Rightarrow 30$$

$$n = 10$$

$$\therefore V_{AB} \Rightarrow 10V \text{ (Ans)} \text{ (Ans)}$$

2nd September, 2021
lecture 4

⇒ Light Emitting Diode (LED) :-


A light emitting diode is simply a forward biased p-n junction which emits spontaneous light radiation. When forward bias is applied, the electron and holes at the junction recombine and energy released is emitted in the form of light for visible.

radiation phosphorous doped GaAs

is commonly used. The advantage of LEDs are -

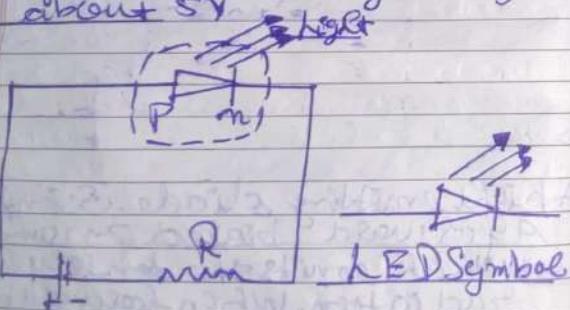- (i) Low operational voltage and less power
- (ii) Fast action with no warm up times.
- (iii) Emitted light is nearly monochromatic.
- (iv) They have long life.



The characteristics of LED are similar to that of Si junction diode but the threshold voltage are much higher and slightly different for each colour. The reverse breakdown voltages of LEDs are very low, about 5V.



⇒ Photodiode

It is a reversed biased P-n junction, illuminated by Radiation. When a p-n junction is reversed biased with no current, a very small reverse saturated current flows across the junction called the dark current. When the junction is illuminated with light, electron-hole pairs are created at the junction due to which additional charge carriers begin to flow across the junction. The current is solely due to minority charge carriers.

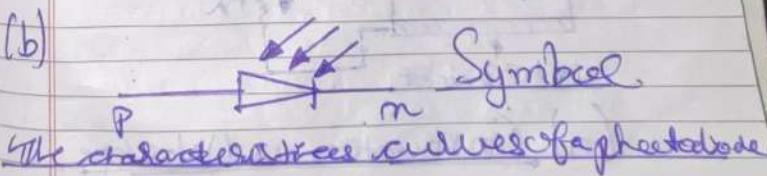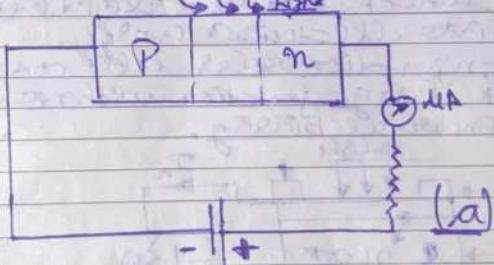
(i) Photodiode is used to measure light intensity because reverse bias current increases with increase of intensity of light.



The characteristic curves of a photodiode

for two different voltages

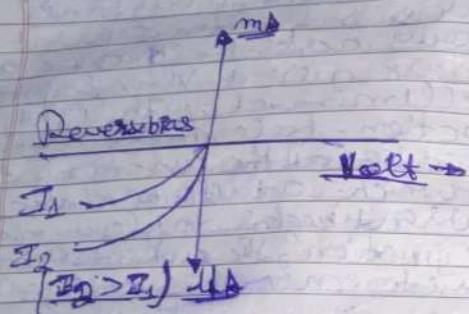
I_1 and I_2 ($I_2 > I_1$) are shown figure



Solar Cell

A solar cell is a junction diode which converts light energy into electrical energy.

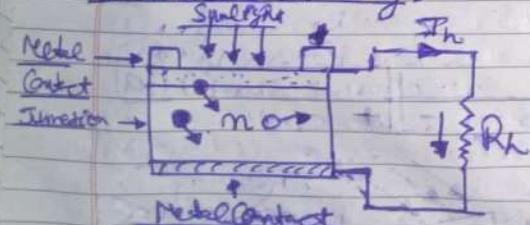A P-n junction solar cell consists of a large junction with no internal biasing.



(a) Construction and Working

Symbol



Surface layer of p-region is made very thin so that the incident photons may easily penetrate to reach the junction which is the active region. To operate in the photovoltaic mode, the generation of photocurrent due to bombardment of optical photons; the materials suitable for photovoltaic are silicon (Si), gallium Arsenide (GaAs), cadmium Sulphide (CdS) and cadmium Selenide (CdSe).

Working: When photon of energy greater than band gap ($h\nu > E_g$) falls on the junction, electron-hole pairs are created which move in opposite direction due to junction field. These are collected at two sides of junction thus producing photo voltage. This gives rise to photo current. Solar cell are used in satellites to recharge their batteries.

(a) Reverse Breakdown

If the reverse bias voltage is made too high, the current through the PN junction increases rapidly at V_R . The voltage at which this happens is called breakdown voltage or Zener Voltage.

(a) Zener Breakdown: - When reverse bias is increased the electric field at the junction also increases. At some stage the electric field becomes so high that it breaks the covalent bonds creating electron, hole pairs. Then a large number of carriers are generated. These carriers a large current flows. This mechanism is known as Zener Breakdown.

(b) Avalanche Breakdown: - At high reverse bias voltage due to high electric field, ionizing charge carriers while crossing the junction move very high velocities. These big collision breaks down the covalent bonds generating more carriers. A chain reaction is established, giving rise to high current. This is called

Avalanche Breakdown

Semiconductor \rightarrow lightly Doped with thin depletion layer

Zener Breakdown

Where covalent bonds of depletion layer is self broken due to high electric field of very high reverse bias voltage.

This phenomenon

Predominant

- At low voltage after "breakdown"
- In P-N having "high Doping"
- P-N junction having thin Depletion layer

Here P-N damage permanently

"In D-C voltage stabilized zener phenomenon is used".

Avalanche Breakdown

Here covalent bonds of depletion layer are broken by collision of "minerals" which acquires high KE from high Electric Field.

This phenomenon

Predominant

- At high voltage after break down
- In P-N having "low Doping"
- P-N junction having thick depletion layer

Here P-N damage permanently due to "heating effect" due to abrupt increase of minerals during repetitive collisions.

\Rightarrow Zener Diode

A zener diode is a specially designed heavily p-n junction having a very

Han depletion layer and having a


PAGE NO.

very sharp breakdown voltage.
It is always operated in breakdown
region. Its breakdown voltage V_Z is
less than 6V.

Zener Diode as a Voltage Regulator

Zener diode may be used as a
voltage regulator. The circuit of
Zener-Diode is shown in figure.

Key in Depletion Layer

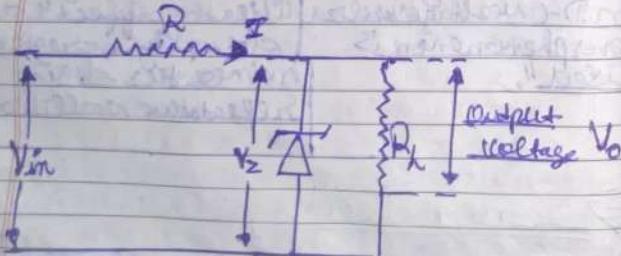


In breakdown region the equation

$$V_o \Rightarrow V_Z \Rightarrow V_{in} - IR$$

DATE / 20
PAGE NO.

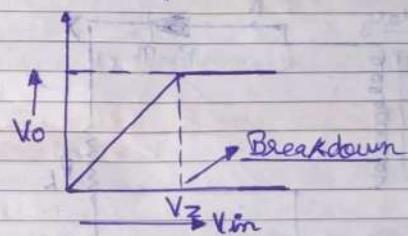Clearly when the input voltage exceeds
zero voltage to keep the voltage
regularly, the extra input voltage
appears across series resistance
Q. The voltage regulation curve
is shown in figure.




⇒ Junction Diode as Rectifier

A rectifier is a device which converts
an alternating current (or voltage)
into a direct (or unidirectional)
current (or voltage). A P-N junction
diode can work as an excellent
rectifier. It offers a low resistance for
the current to flow when it is in
forward bias, but a very high
resistance upon in Reverse Bias.
Thus, it allows current. Thus, it allows
current through it only when forward
biased as a rectifier. The junction
diode can be used either as a half-wave
rectifier or as a full-wave

rectifier

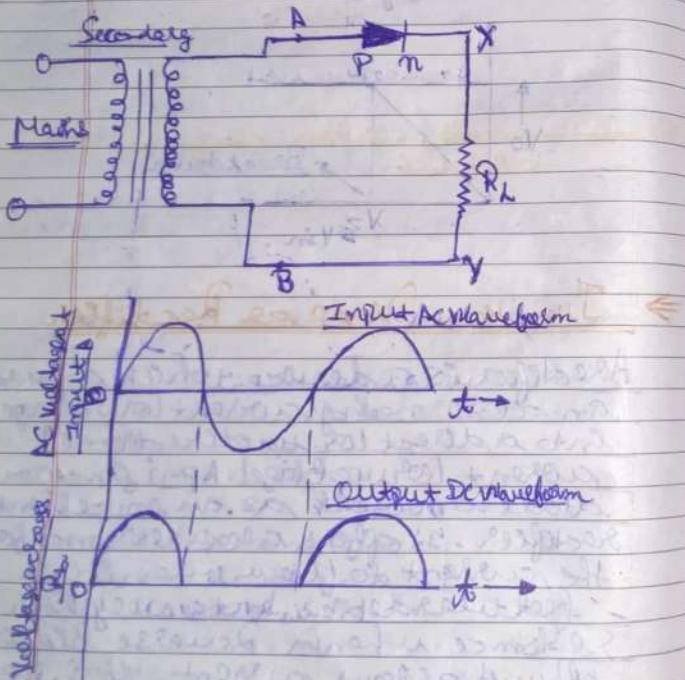(i) p-n junction diode as half-wave rectifier

A simple rectifier circuit called the half-wave rectifier using only one diode.



is negative, the diode is reverse biased and does not conduct.




Since the diode conducts only in the positive half cycles, the voltage between X and V_o or across R_L will be DC but in pulses. When this is given to a circuit called filter [normally a capacitor], it will smoothen the pulsations and will produce a softer steady DC voltage.

(ii) p-n Junction diode as full-Wave rectifier

Two diodes are used for this purpose. The secondary coil of the transformer is wound in two opposite ends and the junction is called a Centre-Tap (CT). During one-half cycle D_1 is forward biased and then D_2 is reversed biased. Therefore D_1 conducts but D_2 does not, current flows from X to Y through load resistance R_L . During another half cycle D_2 is forward biased and D_1 is reverse biased. Therefore D_2 conducts and D_1 does not. In this half cycle also current through D_2 flows from Y to X. Thus current through R_L in both the half cycles is in one direction ie from X to Y.

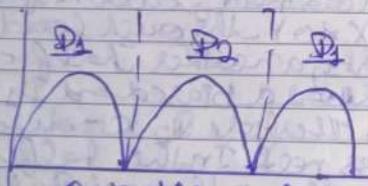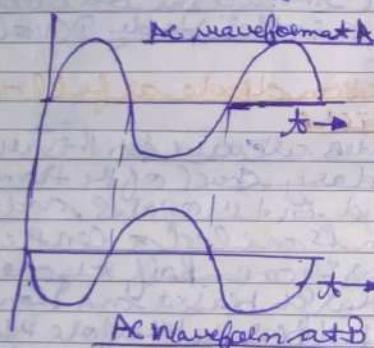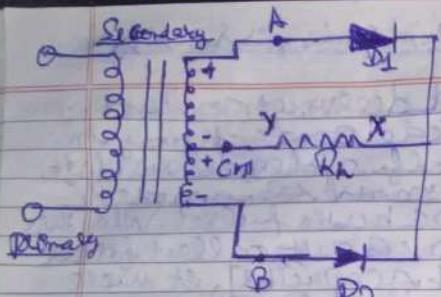(a) Full Wave Rectifier

When the voltage at P is positive, the diode is forward biased and then it conducts and in turn the voltage at P



Transistor

3rd Sept, 2021
Lecture 5



Transistor is a three terminal device which transfers a signal.

from low resistance circuit to high resistance circuit.

This formed when thin layer of one type of intrinsic semiconductor (P or N type) is sandwiched between two thick layers of other type of intrinsic semiconductor.

Each Transistor have three terminals which are:-

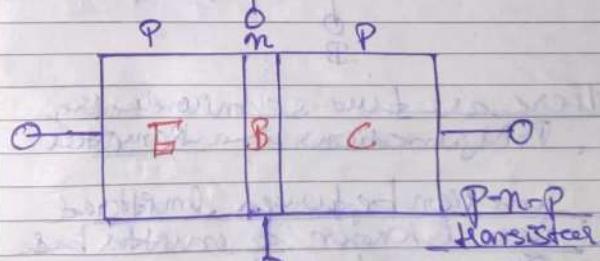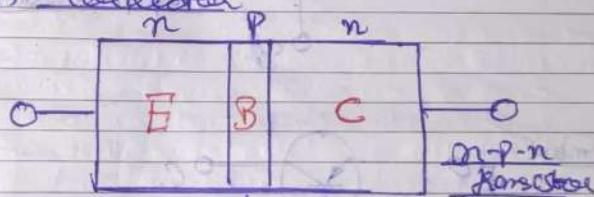- (i) Emitter
- (ii) Base
- (iii) Collector




Transistor have:-


- (1) 2 PN Junction
- (2) It is also called as Diode
- (3) It is also known as Bipolar Junction Transistor (BJT)

- (4) Middle region is lightly doped and it's very thin = Base
- (5) Emitter side is heavily doped.
- (6) Collector has physically large region and moderately doped

Symbol

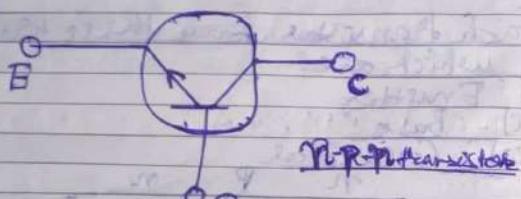

Symbol

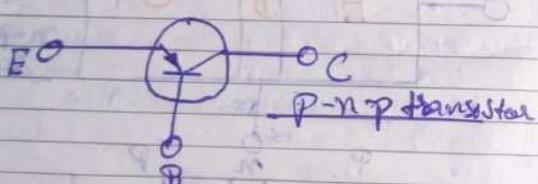


Where are two semiconducting P-N junctions in a transistor?

- (i) Junction between Emitter and Base is known as emitter-base junction (J_{EB}).
- (ii) Junction between base and collector is known as base-collector junction (J_{CB})

- i. In normal operation E-B junction is Forward Biased.
- ii. In normal operation B-C junction is in Reverse Bias.
- iii. For Biasing two battery are required.

3 terminal

Input \Rightarrow 2 terminal	i.e. Terminal must be common
Output \Rightarrow 2 terminal	

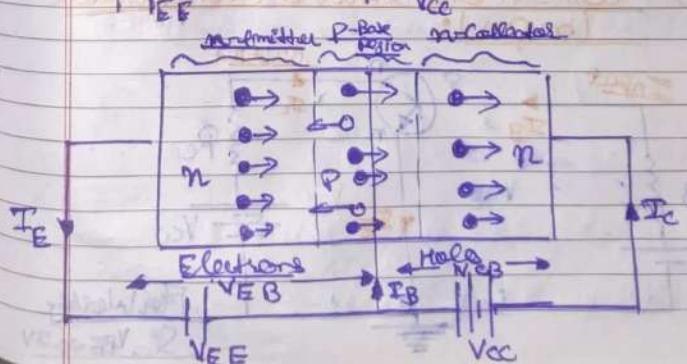

Sohm Base Base is Common

For both

$$I_E = I_B + I_C$$

$$I_E \gg I_B$$


$$I_C \gg I_B$$

and $I_E \approx I_C$ (Almost)

$$I_C = 0.95 I_E \text{ or } 0.99 I_E \text{ (depends on doping)}$$

Emitter emits large number of charge carriers in the base region. Most of these cross over the thin base region and make collector current and some of the carriers injected make base current.

Common Emitter Configuration (npn)

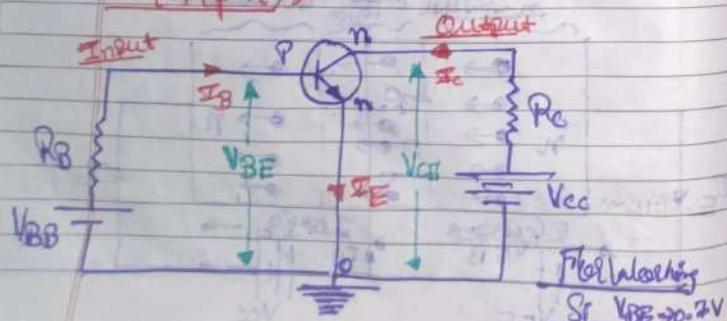

Sohm $V_{CE} > V_{BB}$ (To make collector junction ²⁰ reverse biased)

$$I_E = I_B + I_C \text{ (Always true)}$$

$$\therefore I_C \approx I_E$$

$$I_B \ll I_E \text{ and } I_B \ll I_C$$

Current amplification factor $= \beta = \frac{I_C}{I_B}$

So: $\beta \approx 20 \text{ to } 200$ (Value)

$$\therefore L \Rightarrow \frac{I_C}{I_E} \approx 0.98 \text{ to } 0.99 \text{ (Value)}$$

Equations

$$I_E \Rightarrow I_B + I_C$$

$$\frac{I_E}{I_C} \Rightarrow \frac{I_B}{I_C} + 1$$

$$\frac{1}{\beta} = \frac{1}{I_C} + 1 \quad \boxed{\text{Important Result}}$$

$$\Rightarrow V_{BE} \Rightarrow V_{BB} - I_B R_B \quad \text{--- (1)}$$

$$V_{CE} \Rightarrow V_{CC} - I_C R_C \quad \text{--- (2)}$$

$$R_E \Rightarrow \frac{\Delta V_{BE}}{\Delta I_B} \quad \text{At } V_C = \text{constant}$$

(Dynamic
Resistance
Input)


$$R_O \Rightarrow \frac{\Delta V_{CE}}{\Delta I_C} \quad \text{At } I_B = \text{constant}$$

(Dynamic
Resistance
Output)


Transconductance :-

$$g_m \rightarrow \frac{\Delta I_C}{\Delta V_{BE}}$$

Input Characteristics curve

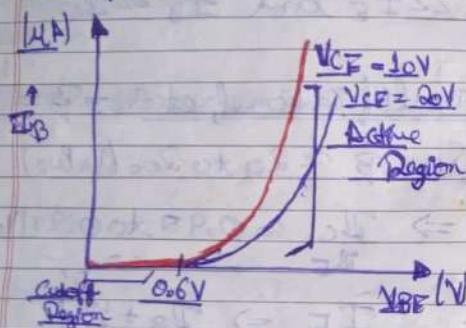

Output Characteristics Curve

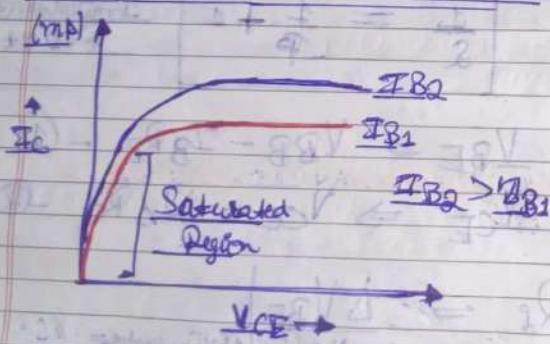


Cutoff Region \rightarrow Base-emitter junction is not properly forward biased

Active Region :- $B.E = \text{Forward Bias}$
 $B.C \Rightarrow \text{Reverse Bias}$

Saturated Region :- Base-collector junction is not properly reverse biased.

4th Sept 2021
lecture # 6

Transistor as Amplifier :-

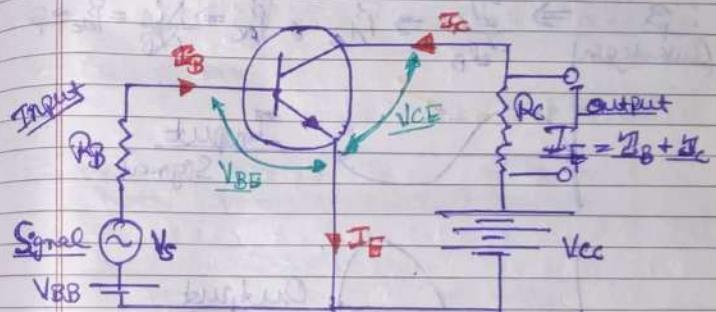

In Active mode

$$V_{BE} \rightarrow V_{BB} + V_s - I_B R_B$$

$$V_{CB} = V_{CC} - I_C R_C$$

$$\therefore \Delta V_{BE} \Rightarrow \Delta V_{BB} + \Delta V_s - R_B \Delta I_B$$

In Active mode $\Delta V_{BE} = 0$ and $\Delta V_{BB} = 0$ (Due to Constant V. Due to)

$$\therefore \Delta V_s \Rightarrow R_B \Delta I_B$$



$$\Delta V_{CE} = \Delta V_{CC} - R_C \Delta I_C \rightarrow A_V$$

Voltage amplification factor (A_V)

$$A_V \rightarrow \frac{\Delta V_O}{\Delta V_I} \Rightarrow -(\beta) \frac{R_C}{R_B}$$

Voltage gain \rightarrow Current gain \times Resistance gain
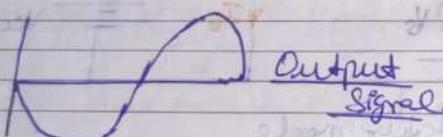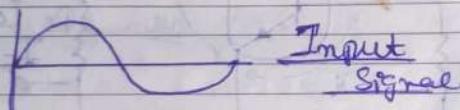
$$\because \beta \cdot \frac{I_C}{I_B} \Rightarrow \beta_{dc} \cdot \beta_{ac} \Rightarrow \frac{\beta_{dc}}{\beta_{ac}} = \beta \Rightarrow A_V = \beta \cdot \frac{R_C}{R_B}$$




Phase Difference between Input Signal Voltage and Output Signal Voltage
 $\rightarrow \pi \Rightarrow 180^\circ$

Power Gain \Rightarrow Voltage gain \times Current gain
 $\Rightarrow -\beta \frac{R_C}{R_B} \times \beta$

Power Gain $\Rightarrow -\beta^2 \frac{R_C}{R_B}$ (Resistance Gain)

Transistor as Switch

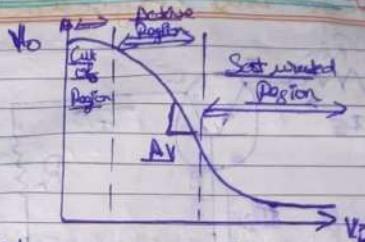

$$V_O = V_{CC} - I_C R_C$$

If $V_i \uparrow I_B \uparrow \text{and } I_C \uparrow \text{and } V_O \downarrow$

- Cutoff Region

$V_O = \text{high}$ $V_i = \text{low}$

- Active Region
Both Properly Biased

- Saturated Region
 $V_O = \text{low}$ $V_i = \text{high}$

Emitter-Base

Forward Biased

Reverse Biased

Reverse Biased

Forward Biased

Collector-Base Pair Working

Forward Biased Active


Reverse Biased Invert

Forward Biased Active

Reverse Biased Cutoff

Forward Biased Saturation

(i) Common-base configuration

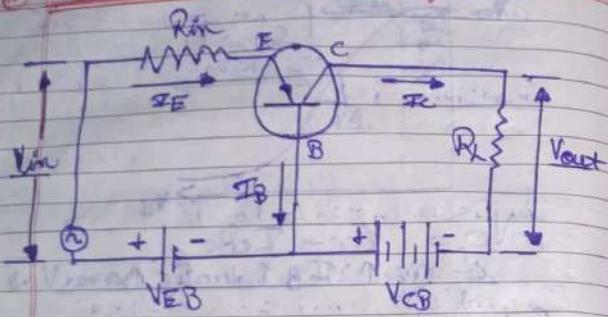

(i) Input current = I_E

(ii) Input Voltage $\Rightarrow V_{EB}$

(iii) Output Voltage $\Rightarrow V_{CB}$

(iv) Output Current $\Rightarrow I_C$

With small increase in emitter-base voltage V_{EB} , the emitter current I_E increases rapidly due to small input resistance.

(v) Input characteristics:



If V_{EB} = Constant, curve between I_C and V_{EB} is known as Input characteristic. It is also known as emitter characteristic.

Dynamic Input Resistance of transistor is given by:


$$R_i \Rightarrow \left(\frac{\Delta V_{EB}}{\Delta I_E} \right) \text{ } V_{CB} = \text{constant}$$

{ R_i is of order of 100Ω }

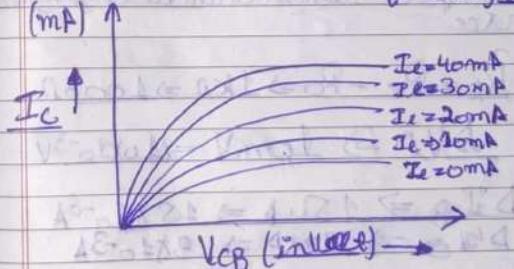(vi) Output characteristics: Making the emitter current I_E constant, the curve between I_C and V_{CB} are known as output characteristics.

Dynamic Output Resistance

$$R_o \Rightarrow \left(\frac{\Delta I_C}{\Delta V_{CB}} \right) I_E = \text{constant}$$



Transistor as CB. Amplifier

(1) AC current gain $A_C \Rightarrow \frac{\Delta I_C}{\Delta I_E}$

(2) DC current gain β_{DC} (or β) $\Rightarrow \frac{\text{Collector current (I_C)}}{\text{Emitter current (I_E)}}$

β_{DC} lies between 0.95 to 0.99 (Value)

(3) Voltage gain $A_v \rightarrow \frac{\Delta V_o}{\Delta V_i}$

$$\Rightarrow A_v \rightarrow S_{ac} \times \text{Resistance gain}$$

(4) Power gain $\rightarrow S_{ac} \times \text{Resistance gain}$

Q4: An NPN transistor is used in common emitter configuration as an amplifier with $1\text{k}\Omega$ load resistance. Signal voltage of 10mV is applied across the base-emitter. This produces a 3mA change in the collector current and $15\mu\text{A}$ change in the base current of the amplifier. The input resistance and voltage gain are

$$R_i = R_e = R_o \Rightarrow 1\text{k}\Omega \Rightarrow 1000\Omega$$

$$\Delta V_i \Rightarrow 10\text{mV} \Rightarrow 10 \times 10^{-3}\text{V}$$

$$\Delta I_B \Rightarrow 15\mu\text{A} \Rightarrow 15 \times 10^{-6}\text{A}$$

$$\Delta I_C \Rightarrow 3\text{mA} \Rightarrow 3 \times 10^{-3}\text{A}$$

$$\Delta V_i \Rightarrow R_B \Delta I_B$$

$$\frac{10 \times 10^{-3}}{2 \times 10^3} \Rightarrow R_B \times 15 \times 10^{-6}$$

$$\frac{1}{3} \Rightarrow R_B$$

$$0.67\text{k}\Omega \Rightarrow R_B$$


Voltage gain $\Rightarrow \frac{\Delta V_o}{\Delta V_i} \times \frac{R_c}{R_B}$

$$\Rightarrow 3 \times 10^{-3} \times \frac{1000 \times 3}{2 \times 10^3}$$

Voltage gain $\Rightarrow 10^{-3} \times \frac{3}{2}$

Voltage gain $\Rightarrow 300$

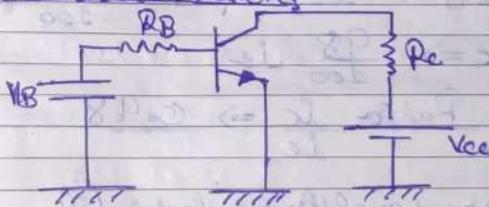Q3: A common emitter amplifier circuit built using an n-p-n transistor is shown in the figure. It's collector current + gain is $250 \times R_c = 1\text{k}\Omega$ and $V_{cc} \Rightarrow 10\text{V}$. What is the minimum base current for V_{ce} to reach saturation?



Ans Q3: $\beta \Rightarrow 250 = \frac{I_c}{I_B}$

$$R_c \Rightarrow 1\text{k}\Omega \Rightarrow 1000\Omega$$

$$V_{cc} \Rightarrow 10\text{V}$$

$$250 = \frac{10^2}{I_B}$$

$$V_{ce} \Rightarrow V_{cc} - I_c R_c$$

$$V_{cc} \Rightarrow I_c R_c$$

$$10 = 1000 \times I_c$$

$$10^{-2} \Rightarrow I_c$$

$$I_B \Rightarrow \frac{1}{25000}$$

Ans 4A

Q4: In an N-P-N transistor DATA PAGE NO. 10

Electrons entering emitter in 10^{-6} s. 2% of the electrons are lost in the base. Calculate current transfer ratio and current amplification factor.

$$\text{Ans} - i_e = \frac{m_e}{t} = \frac{10^{10} \times 1.6 \times 10^{-19}}{10^{-6}} = 1.6 \times 10^{-3} \text{ A}$$

$$i_e \Rightarrow 1.6 \times 10^{-3} \text{ A}$$

$$i_B = 2\% \text{ of } i_e = \frac{2}{100} \text{ of } i_e$$

$$i_c \Rightarrow \frac{98}{100} i_e$$

$$\therefore (i) \text{ Ratio } \frac{i_c}{i_e} \Rightarrow 0.98$$

(ii) Current amplification factor (β)

$$\beta \Rightarrow 49 \quad (\text{Ans})$$

Q5: A transistor is connected in common-emitter (CE) configuration. The collector supply is 2V and a voltage drop across a resistor of 800Ω in the collector circuit is 0.5V. If the current gain factor (α) is 0.96, find base-current.

$$\frac{1}{2} + \frac{1}{B} + 1$$

$$1 = \frac{1}{B} + 1$$

$$100 - 96 \Rightarrow \frac{1}{B} \Rightarrow \frac{96}{4}$$

$$\therefore \beta \Rightarrow 24$$

$$\text{Sol: } V_C \Rightarrow 0.5 \text{ V} \Rightarrow \frac{9}{800} \text{ Ampere}$$

$$\beta = \frac{i_c}{i_B} \quad i_B \Rightarrow \frac{i_c}{\beta}$$

$$I_B \Rightarrow \frac{9 \times 10^{-3}}{8 \times 24} \Rightarrow 264 \text{ A}$$

Q6: In a Transistor:-

Ans 46: (c) Base has least concentration of impurity.

Q7: The thinnest part of transistor is:-

Ans 47: (2) Base.

Q8: A N-P-N transistor conducts in:-

Ans 48: (B) Collector is positive and emitter is negative with respect to base.

Q9: You use transistor as an amplifier.

Note (1) Emitter base junction

forward biased and collector junction is reverse biased.

Sol: In a N-P-N transistor circuit, the collector current is 10mA. If 90% of the electrons reach the collector from the emitter, current (I_E) and base current (I_B) are given by

$$\text{Ans} \quad I_C \Rightarrow 10 \text{mA} \Rightarrow 10 \times 10^{-3} \text{A}$$

$$\text{So: } 90\% I_E = I_C$$

$$\frac{90}{100} \times I_E \Rightarrow 10 \times 10^{-3}$$

$$I_E \Rightarrow \frac{1}{90}$$

$$I_E \Rightarrow 0.11 \times 10^{-3}$$

$$I_B = 11 \text{mA}$$

$$\text{So: } I_B = I_E + I_C$$

$$11 \Rightarrow I_B + 10 \text{mA}$$

$$[1 \text{mA} = I_B] \text{ Answer}$$

Sol: When N-P-N transistor is used as an amplifier:

Ans (4) Voltage more from base to emitter

Sol: Which of the following is true?

Ans (1) Common emitter is commonly used because current gain is maximum.


Ans (2) Transistor relation in current amplification factor is:

$$\frac{1}{2} - 1 = \frac{1}{B}$$

$$\frac{1}{2} \Rightarrow \frac{B+1}{B}$$

$$\boxed{\frac{1}{2} \Rightarrow \frac{B}{B+1}} \quad \boxed{\frac{1}{2} = \frac{1}{B}}$$

Sol: Two junction diodes of one of germanium (Ge) and other of silicon (Si) are connected as shown in figure to a battery of 12V and a load resistance of 10kΩ. The germanium diode conducts at 0.3V and silicon diode at 0.7V. When a current flows in the circuit, the potential (in V) of terminal Y will be-

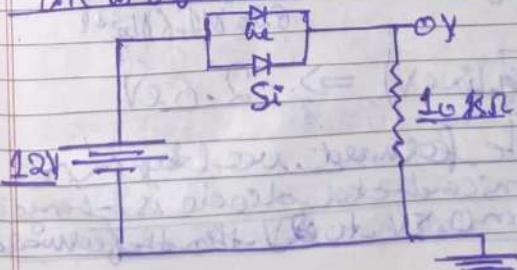

Ans 54: So both the Diodes will be forward biased. Some minimum resistance is minimum. So it will go through a path of less.

$$\text{The potential V of } V = 12 - 0.3 \Rightarrow 11.7 \text{ Volt}$$

Q5: When light falls on a p-n junction diode, its conductivity increases. Experimentally it is found that the conductivity changes only when the wavelength of the incident light is less than 600 nm. This is called the photoelectric effect.

Ans 55: So, $Eg \Rightarrow hc$

$$Eg \Rightarrow \frac{6.626 \times 10^{-34} \times 3 \times 10^8}{620 \times 10^{-9}}$$

$$Eg \Rightarrow \frac{19.8 \times 10^{-17}}{620 \times 1.6 \times 10^{-19}}$$

$$Eg(\text{line}) \Rightarrow 2.0 \text{ eV}$$

56: If the forward voltage on a semiconductor diode is changed from 0.5 V to 0.8 V, then the forward current changes by 1.5 mA. Find the forward resistance (kR) of the diode.

current changes by 1.5 mA. $\Delta I = 1.5 \text{ mA}$

forward resistance (kR) of the diode will be

$$\text{Ans 56: } R_f \Rightarrow \frac{\Delta V}{\Delta I}$$

$$\Delta V \Rightarrow 0.8 - 0.5 \Rightarrow 0.3 \text{ V}$$

$$\Delta I \Rightarrow 1.5 \text{ mA}$$

$$R_f \Rightarrow \frac{0.3}{1.5 \times 10^{-3}} \Rightarrow 200 \Omega$$

$$R_f \Rightarrow 1 \text{ k}\Omega$$

Sol: When the reverse potential in a semiconductor diode are 10 V and 20 V then the currents depending on reverse currents are $20 \mu\text{A}$ and $5 \mu\text{A}$ respectively. Reverse resistance (kR) of junction diode will be

$$\text{Ans 57: } R_R \Rightarrow \frac{\Delta V}{\Delta I}$$

$$R_R \Rightarrow \frac{20}{20 \times 10^{-6}} \Rightarrow 2 \times 10^6 \Omega$$

$$R_R \Rightarrow 4 \times 10^9 \Omega$$

$$\text{or } 400 \text{ k}\Omega \text{ (Ans)}$$


Ans 58: If the frequency of input alternating current is 50 Hz, then the ripple

frequency (Hz) of output
percentage of full wave
rectifier voltage

Ans 58: Output Frequency $\rightarrow 2 \times$ Input frequency.

$$\text{Ripple frequency} \rightarrow 2 \times 50 \text{ Hz} \\ \Rightarrow 100 \text{ Hz}$$

59: The current (mA) flowing through the zener diode is

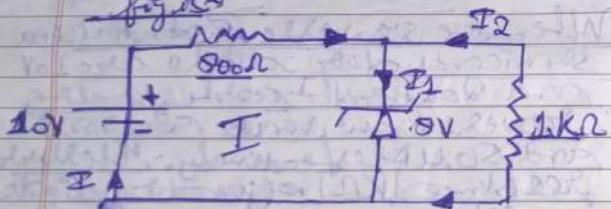

Ans 59: Zener Voltage $\rightarrow 5V$

Input current in zener branch $\rightarrow I_1$
and current in load $\rightarrow I_2$

From KVL: $V_{\text{zener}} \Rightarrow V_{\text{zener}}$

$$I_2 \times 1 \times 10^3 \Omega \Rightarrow 5V$$

$$I_2 \Rightarrow 5 \text{ mA}$$

loop law in "I"

$$10 - 500I - 5 = 0$$

$$10 = 500I + 5 \\ 10 - 5 = 500I \\ 10 \times 10^{-2} \Rightarrow I$$

$$\text{Ans 60: } I = I_1 + I_2$$

$$\frac{10}{100} - \frac{5}{1000} \Rightarrow I_1 \\ 10 \text{ mA} - 5 \text{ mA} = I_1$$

$$\therefore I_1 \Rightarrow 5 \text{ mA (Answe)}$$


60: The depletion layer in silicon diode is $1.51 \mu\text{m}$ wide and it knees at 150.6 V . If the electric field in the depletion layer is $2 \times 10^5 \text{ V/m}$, find

$$\text{Ans 60: } E \Rightarrow \frac{V}{d}$$

$$E \Rightarrow \frac{150.6}{1.51 \times 10^{-6}} \\ E \Rightarrow 6 \times 10^5 \text{ V/m}$$

$$\therefore d \Rightarrow 6 \text{ (Answe)}$$


61: In the circuit given below, the value of the current (in mA) is

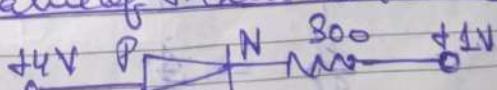

Ans 61:

Since $V_D > V_B$ So

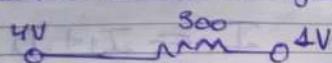It is in forward bias and
at ideal condition it
behaves as a straight line



$$I \Rightarrow \frac{\beta}{300} \Rightarrow 10mA$$

Ques 62: If load resistance $R = 0.9$, then value
of $\beta = ?$

$$\frac{1}{0.9} = \frac{1}{\beta}$$

$$\frac{10-9}{9} = \frac{1}{\beta}$$

$$\therefore \beta \Rightarrow 9 \text{ (Answer)}$$

Ques 63: In a P-N-P transistor working
as a common-base amplifier
current gain is 0.96 and emitter
current is 7.2 mA. The base
current (mA) is:

Ans 63:

$$S = 0.96$$

$$\frac{1}{0.96} - 1 = \frac{1}{\beta}$$

$$\frac{4}{96} = \frac{1}{\beta}$$

$$\therefore \beta \Rightarrow \frac{96}{4} \Rightarrow 24$$

Also: $S \Rightarrow \frac{I_C}{I_E}$

$$\frac{0.96}{100} \Rightarrow \frac{I_C \times 10}{7.2 \times 10^{-3} A}$$

$$\frac{96}{100} \Rightarrow \frac{I_C}{7.2} \times 10^4$$

$$I_C \Rightarrow \frac{96 \times 7.2}{10^4} \text{ Amperes}$$

Ans:

$$\beta \Rightarrow \frac{I_C}{I_B}$$

$$24 \Rightarrow \frac{96 \times 7.2}{10^4 \times I_B}$$

$$I_B \Rightarrow \frac{288 \times 10^{-3}}{10^3}$$

$$I_B \Rightarrow 0.288 \text{ mA}$$

$$I_B \Rightarrow 0.29 \text{ mA (Answer)}$$

Ques 64: In the fig., a common-emitter
configuration of N-P-N transistor
with current gain $\beta \Rightarrow 100$ is used.
The output voltage (in V) of the
amplifier will be:-



Ans64: Sol. $V_{BE} \Rightarrow I_B \times R_B$

$$1 \times 10^{-3} = I_B \times 1 \times 10^3$$

$$10^{-6} = I_B$$

Now $\beta = \frac{I_C}{I_B}$

$$100 = \frac{I_C}{I_B}$$

$$I_C \Rightarrow 100 \times 10^{-6}$$

$$I_C \Rightarrow 10^{-4}$$

Sol:- $V_{CE} \Rightarrow V_o \Rightarrow I_C R_C$

$$V_o \Rightarrow 10^{-4} \times 10 \times 10^3$$

$$\Rightarrow 10^{-4} \times 10^4$$

$$V_o \Rightarrow 1 \text{ Volt (Answe)}$$

Q5: In an N-P-N transistor the values of base current and collector current are 10 mA and 9 mA respectively. The emitter current is I_E .

$$I_E = I_B + I_C$$

$$I_B \Rightarrow 10 \times 10^{-3} + 9 \times 10^{-3}$$

$$I_E \Rightarrow \frac{90}{10} = 9.01 \times 10^{-3}$$

$$I_E = 9.01 \text{ mA } (\text{Answe})$$

DATE : / /
PAGE NO.

66:

In a common emitter circuit
If V_{CE} is changed to 0.2 V then
collector current changing by
 $4 \times 10^{-3} \text{ mA}$ (Output level 8 kV)

Ans65:-

$$\Delta V_{CE} \Rightarrow \Delta I_C R_C \quad (\text{Reqd})$$

$$\frac{0.2}{10} \Rightarrow 4 \times 10^{-3} \times 10^{-3} \times R_C$$

$$\frac{1}{2} \times \frac{1}{2 \times 10^{-5}} = R_C$$

$$\frac{0.5 \times 10^{-4}}{5 \times 10^{-4}} \Rightarrow R_C$$


\therefore Resistance Output $\Rightarrow 80 \text{ k}\Omega$ (Answe)

5th Sept 2021
Lecture 7

\Rightarrow logic Gate.

① Analog Signal

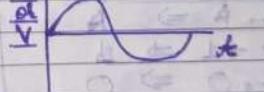\Rightarrow It's a continuously varying Signal (current or voltage). i.e.



② Digital Signal

It can have only two discrete values High or Low

